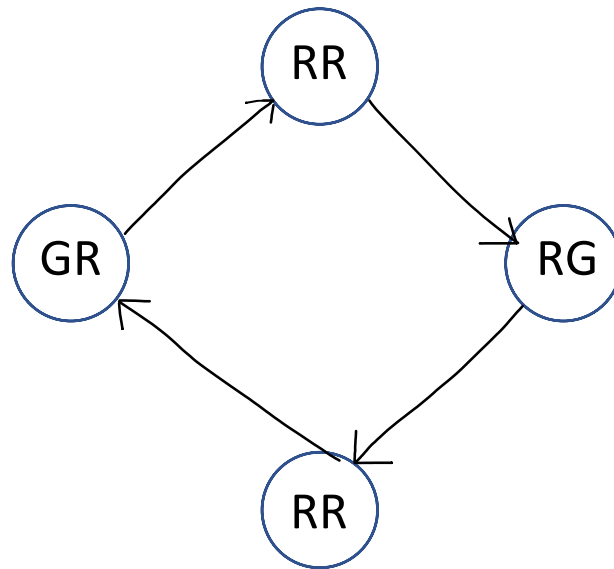


Part 2: (a) State Diagram for the System

(Draw a state diagram as in page 5)



A Four-State Design

Notation: L1L2, so GR = Light 1 is Green and Light 2 is Red

Part 2: (b) Define the State Table

(Complete a state table as in page 6)

Present State		Next State	
Number	Alias	Number	Alias
0	GR	1	RR
1	RR	2	RG
2	RG	3	RR
3	RR	0	GR

Part 2: (c) Derive the Output Equations.

(Derive output equations (for the lights) as in page 10)

	Alias	$Q_1 Q_0$	G1	R1	G2	R2
0	GR	0 0	1	0	0	1
1	RR	0 1	0	1	0	1
2	RG	1 0	0	1	1	0
3	RR	1 1	0	1	0	1

Output equations

$$G1 = Q_1' \bullet Q_0'$$

$$G2 = Q_1 \bullet Q_0'$$

$$R1 = G1'$$

$$R2 = G2'$$

Part 2: (d) Derived the State Transition Table.

(Complete a state transition table as in page 12)

Present State		Next State	
	Q ₁ Q ₀	Q ₁ Q ₀	
0	0 0	0 1	
1	0 1	1 0	
2	1 0	1 1	
3	1 1	0 0	

Part 2: (e) Derive the Input Equations

(Derive the input equations (J-K inputs) as in page 16)

Separating the Table into Two Tables

Q ₁		Q ₀	
PS	NS	PS	NS
Q ₁ Q ₀	Q ₁	Q ₁ Q ₀	Q ₀
0 0	0	0 0	1
0 1	1	0 1	0
1 0	1	1 0	1
1 1	0	1 1	0

Deriving the Input Tables

Flip-Flop 1				Flip-Flop 0			
PS	NS	Input		PS	NS	Input	
Q ₁ Q ₀	Q ₁	J ₁	K ₁	Q ₁ Q ₀	Q ₀	J ₀	K ₀
0 0	0	0	d	0 0	1	1	d
0 1	1	1	d	0 1	0	d	1
1 0	1	d	0	1 0	1	1	d
1 1	0	0	d	1 1	0	d	1

Karnaugh Maps for deriving the Input Equations

(1) Karnaugh Map: J₁

Q ₁ \ Q ₀	0	1
0	0	1
1	d	d

$$J_1 = Q_0$$

(2) Karnaugh Map: K_1

$Q_1 \backslash Q_0$	0	1
0	d	d
1	0	1

$$K_1 = Q_0$$

(3) Karnaugh Map: J_0

$Q_1 \backslash Q_0$	0	1
0	1	d
1	1	d

$$J_0 = 1$$

(4) Karnaugh Map: K_0

$Q_1 \backslash Q_0$	0	1
0	d	1
1	d	1

$$K_0 = 1$$

The Input Equations Are:

$$J_1 = Q_0 \qquad J_0 = 1$$

$$K_1 = Q_0 \qquad K_0 = 1$$

Part 2: (f) Draw the Circuit

(Draw the circuit without the D-flipflops as in page 17)

